

ONLINE CONTINUOUS INTERNAL EVALUATION- 3

Dept: FY	Sem / Div:II nd A/B/C	Sub: Basic Electronics	S Code: 18ELN24
Date:25/09/21	Time: 9:30-11:00 AM	Max Marks: 50	Elective:N
Note: Answer any 2 full questions, choosing one full question from each part.			

QN	Questions	Marks	RBT	COs
PART A				
1	a Explain RC phase-shift oscillator with circuit diagram and necessary equations.	9	L2	CO3
	b Define an oscillator. Explain the Barkhausens criteria for oscillations.	8	L2	CO3
	c Perform the following (i) Convert $(ABCD)_{16} = (?)_2 = (?)_8$ (ii) Subtract $(22)_{10} - (17)_{10}$ using 1's and 2's compliment method.	8	L3	CO4
OR				
2	a Explain the operation of IC-555 as an Astable oscillator with neat circuit diagram and necessary equations.	9	L3	CO3
	b With a neat circuit diagram explain the working of Wein-bridge oscillator.	8	L2	CO3
	c What is multiplexer ? Implement 4:1 multiplexer using basic gates.	8	L3	CO4
PART B				
3	a Simplify the following expressions i) $Y=AB+ A'C+ AB'C (AB+C)$ ii) $Y= AB+A(B+C)+B(B+C)$ iii) $Y=(A+B)(A'+B)$	9	L3	CO4
	b Convert the following. i) $(867)_{10} = (?)_2 = (?)_{16}$ ii) $(110111101.01)_2 = (?)_{10} = (?)_{16}$	8	L3	CO4
	c Design full adder circuit and implement it using basic gates.	8	L3	CO4
OR				
4	a Draw and explain 4-bit shift register.	9	L2	CO4
	b With a neat logic diagram and truth table, explain the working of a JK flip-flop.	8	L2	CO4
	c Explain the basic elements of communication system with block diagram.	8	L2	CO5